

22324

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Illustrate your answers with neat sketches wherever necessary.
(3) Figures to the right indicate full marks.
(4) Assume suitable data, if necessary.
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.
(6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following: 10
- a) Define active power and reactive power for R-L-C series circuit.
 - b) Define RMS value and average value related to sinusoidal AC waveform.
 - c) Define term conductance and susceptance, state its unit.
 - d) Define - Phase sequence and write equations for instantaneous values of 3 ϕ voltages.
 - e) Give equations for delta to star transformation.
 - f) State Norton's theorem.
 - g) State Reciprocity theorem.

P.T.O.

2. Attempt any THREE of the following: **12**

- a) Derive the expression for current in pure inductor circuit when connected to 1 ϕ AC Supply with graphical representation.
- b) Draw and explain RLC parallel Ckt. Find out the equation for resonant frequency.
- c) State any four advantages of polyphase circuit over single phase circuit. (system)
- d) Find the current in 6Ω resistor in the circuit shown in Fig. No. 1 using mesh analysis.

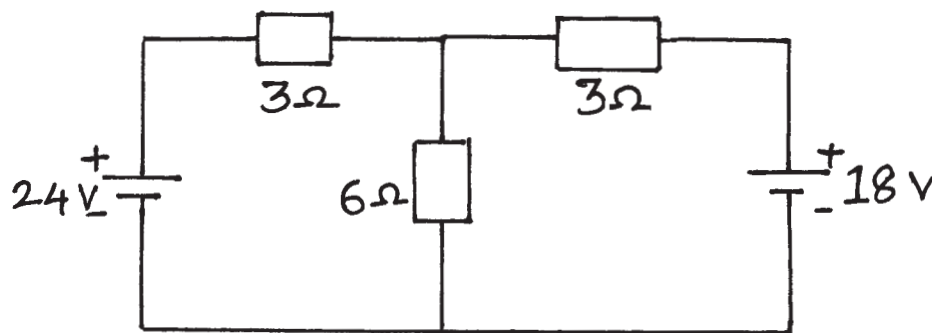


Fig. No. 1

3. Attempt any THREE of the following: **12**

- a) Derive the expression for resonance frequency for a RLC series circuit.
- b) Compare series resonance to parallel resonance on the basis of
 - i) Resonant frequency
 - ii) Impedance
 - iii) Current
 - iv) Magnification
- c) A star connected 3 ϕ load is supplied from 3 ϕ , 415V, 50 Hz supply. If the line current is 20 A and total power taken is 10KW, then determine
 - i) Load resistance and reactance per phase
 - ii) Load power factor
 - iii) Total 3 ϕ reactive power

- d) Find current in 40Ω and 10Ω in Fig. No. 2 using node voltage analysis method.

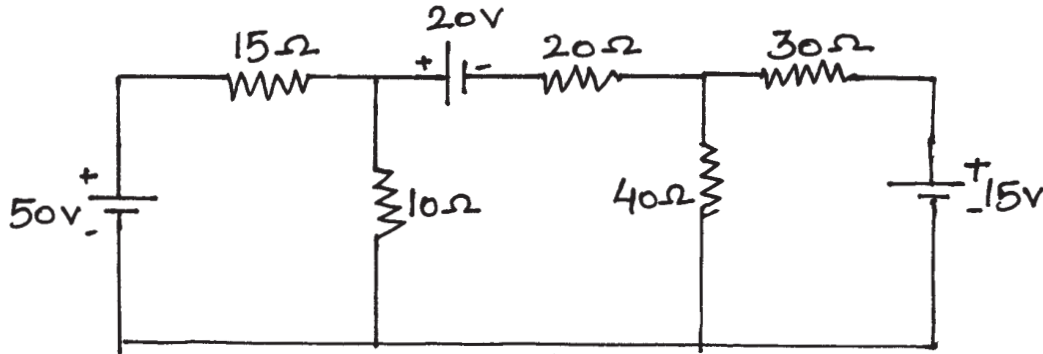


Fig. No. 2

- e) State Norton's theorem. Also write stepwise procedure for applying Norton's theorem to simple Ckt.

4. Attempt any THREE of the following:

12

- a) A R-L-C series circuit with a resistance of 20Ω , inductance of 0.25 H and capacitance of $100\mu\text{F}$ is supplied with 240 V variable a.c. supply, calculate.
 - i) Resonance frequency
 - ii) Current at this condition
 - iii) Power Factor
 - iv) Quality Factor
- b) A choke coil has a resistance of 2Ω and an inductance of 0.0035 H is connected in parallel with $350\mu\text{F}$ capacitor which is in series with a resistance of 20Ω . When the combination is connected across a 200 V , 50 Hz .

Calculate

- i) Total current taken
- ii) P.F. of whole circuit
- c) Each phase of delta-connected load comprise a resistor of 50Ω and capacitor of $50\mu\text{F}$ in series. Calculate the line and phase currents when the load is connected to a 440 V , 3 phase, 50 Hz supply.

- d) Calculate the value of R which will absorb maximum power from the circuit of Fig. No. 3.

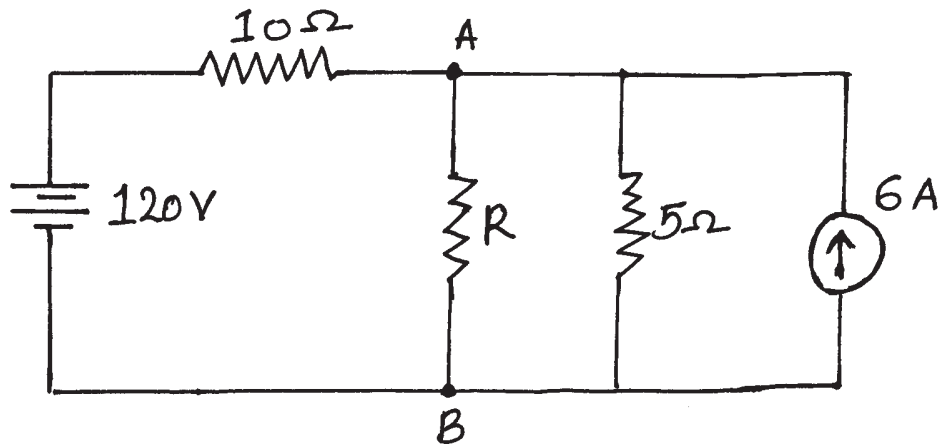


Fig. No. 3

5. Attempt any TWO of the following:

12

- a) A coil having resistance of 10Ω and inductance of 0.15H is connected in parallel with R-C series combination having $R = 5\Omega$ and $C = 20\mu\text{F}$. If supply voltage is 110 V , 50Hz then
- Draw circuit diagram
 - Calculate branch currents using impedance method
 - Power absorbed by the each branch
- b) Reduce the network shown in Fig No. 4 by applying Star/Delta or Delta/Star transformation and determine equivalent resistance ' R_{AB} '.

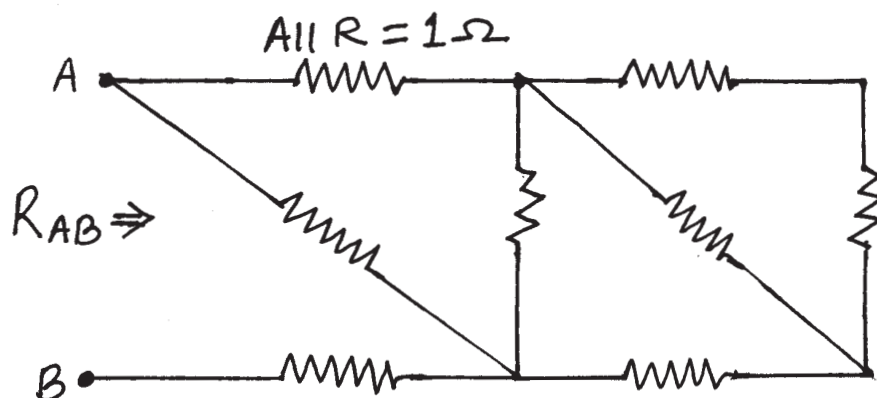


Fig. No. 4

- c) Find I_L for the circuit shown in Fig. No. 5 using superposition theorem.

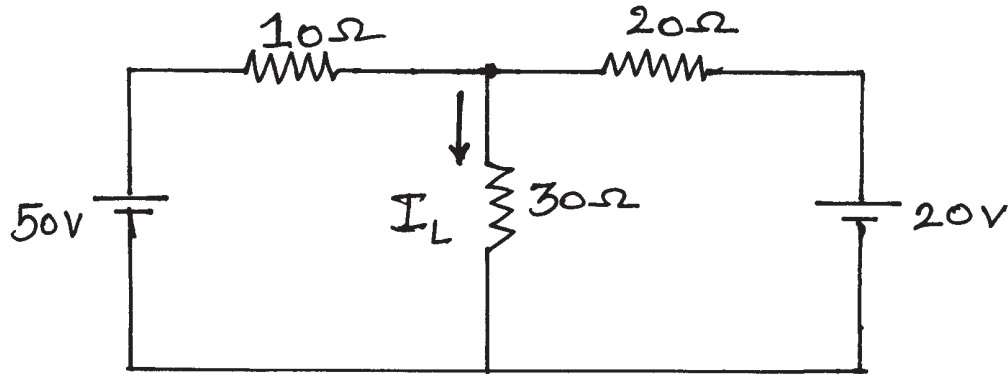


Fig. No. 5

6. Attempt any TWO of the following:

12

- a) An inductive coil $(10+j40)\Omega$ impedance is connected in series with a capacitor of $100\mu\text{F}$ across 230V, 50Hz, 1 ϕ Mains.

Find :

- Current through the circuit
 - P.F of the circuit
 - Power dissipated in the circuit.
 - Draw the phasor diagram.
- b) In a 3 Phase star connected system, derive the relationship $V_L = \sqrt{3} V_{ph}$.
- c) Apply superposition theorem to compute current I in the network shown in Fig. No. 6.

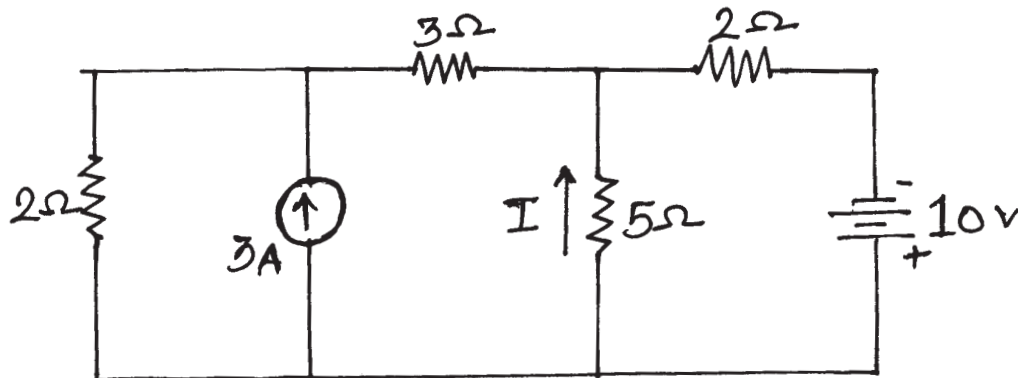


Fig. No. 6