

22421

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE :

10

- (a) State & Explain Duality Theorem.
- (b) Draw symbol & write Truth Table for EX-OR Gate & EX-NOR Gate.
- (c) Convert binary number 1011 into gray number.
- (d) Define min. term & max. term.
- (e) State the function of compiler.
- (f) Identify the addressing mode of the instruction MOV A, @ RO.
- (g) State the function of RS and R/W pin in 16×2 LCD display.

2. Attempt any THREE :

12

- (a) State and verify de-morgan's first and second theorem using Truth Table.
- (b) Compare TTL, CMOS, ECL Logic family on the basis of (1) Fan-out (2) Power dissipation (3) Figure of merit (4) Propagation delay.



- (c) What is Rule around condition in J-K flip flop. Suggest a suitable method to overcome drawback.
- (d) State the need of De-multiplexer. Design 1 : 8 De-multiplexer using 1 : 4 De-multiplexer.

3. Attempt any THREE :

12

- (a) Simplify using K-map and implement using NAND-NAND gate only.

$$Y = \Sigma m (0, 1, 2, 3, 5, 7, 8, 9, 11)$$

- (b) Compare between Micro-processor & Micro controller. (4 points)
- (c) Evaluate the following program and specify the content of accumulator and status of PSW Register after execution :

MOV A, # 23 H

MOV OF OH, # 02 H

MUL AB

END.

- (d) Draw the interfacing diagram of 8 LED connected to port 2 of 8051. Write a program to toggle LED after some delay.

4. Attempt any THREE :

12

- (a) $Y = A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$. Simplify this expression using Boolean rules.
- (b) Design Full Adder with Two half adder and write its Truth Table.
- (c) Draw pin diagram of 8051 and explain function of pin 9, pin 20, 40.
- (d) Which pins of 8051 are used to perform the following function :
 - (i) Receive the serial data
 - (ii) Enable External memory interface.
 - (iii) Multiplexing & De-multiplexing of address / data lines.
 - (iv) Applying External interrupts.
- (e) List addressing mode of 8051 with one example of each.

5. Attempt any TWO :**12**

- (a) Draw block diagram of internal architecture of 8051 and explain function of each block.
- (b) Develop ALP to transfer seven number from internal memory location 20 H to 40 H.
- (c) Draw interfacing diagram of 7 segment display with 8051. Write ALP to display number from 0 to 9.

6. Attempt any TWO :**12**

- (a) Construct 3 bit asynchronous up counter using Flip Flop. Draw it's timing diagram.
 - (b) Describe the memory organization of 8051 microcontroller.
 - (c) Draw a interfacing diagram of stepper motor with 8051. Write ALP to rotate stepper motor in clockwise direction.
-

